

Part IA Digital Electronics Notes

1 K-Map

- Plot all minterms in a grid, indexed using grey code
- Group terms:
 - Having a size equal to a power of 2
 - With groups as large as possible
 - Groups can wrap around corners and edges
- To find the product of sums form, group the zero terms and apply DeMorgan's law
- Plot don't cares as an X and these can be in or outside of a group
- **Cover** - A term covers a minterm when that minterm is part of that term
- **Prime Implicant** - A term that can not be further combined
- **Essential Prime Implicant** - A prime implicant that covers a minterm that no other prime implicant covers
- **Covering Set** - A minimum set of prime implicants which includes all essential terms plus any other prime implicants required to cover all minterms

2 Q-M Method

- List all minterms and don't cares as binary numbers, group based on number of ones
- Compare elements in adjacent groups, if they differ by just one then put into second column, with differing bit blanked out
- Repeat, labelling and unpaired elements with an asterisk
- Make a prime implication chart
 - Label columns with minterms (exclude don't cares)
 - Label rows with those elements with asterisks, and the numbers they could represent
 - Put an X in the locations when there is a cross over, eg. 4 on row and column
- Look for column with only one X in, cross out any minterms in the same row as this lone X
- Find as few primes as possible to cover the remaining crosses

3 Combinational Logic

- Combinational logic circuits have no memory
- An n -level combinational logic circuit has two gates between input and output

3.1 Boolean Algebra

- Commutation

- $a + b = b + a$

- $a.b = b.a$

- Association

- $(a + b) + c = a + (b + c)$

- $(a.b).c = a.(b.c)$

- Distribution

- $a.(b + c + ..) = a.b + a.c + ...$

- $a + (b.c....) = (a + b).(a + c)....$

- Absorption

- $a + a.c = a$

- $a.(a + c) = a$

- DeMorgan's Law

- $\overline{a + b + c + ...} = \bar{a}.\bar{b}.\bar{c}....$

- $\overline{a.b.c....} = \bar{a} + \bar{b} + \bar{c} + ...$

3.2 Normal Forms

- Disjunctive Normal Form

- A boolean function expressed as ORing of its minterms

- Said to be in sum of products form

- Conjunctive Normal Form

- Maxterms are expressions that are only false for one row of a truth table

- The conjunctive normal form is the ANDing of an expressions maxterms

- Said to be in product of sums form

3.3 Hazards

- It takes time for a gate's output to change in response to a change of inputs, this is gate propagation delay

- **Static Hazard** - The output undergoes a momentary transition when one input changes, when it is supposed to remain unchanged

- Solved by adding another term in the K-map, covering overlapping the essential terms

- Do this on complimented k-map for a 0 hazard

- **Dynamic Hazard** - The output changes more than once when it is supposed to change just one

4 Adders

4.1 Half Adder

- Adds together two, single bit binary numbers a and b , has the following equations

$$sum = \bar{a}.b + a.\bar{b}$$

$$c_{out} = a.b$$

4.2 Full Adder

- Adds together two single bit binary numbers with a carry bit, has the following equations

$$sum = \bar{c}_{in}.(\bar{a}.b + a.\bar{b}) + c_{in}.(\bar{a}.b + a.\bar{b})$$

$$c_{out} = b.a + c_{in}.(b + a)$$

4.3 Ripple Carry Adder

- To add two n bit numbers chain together n full adders
- If you compliment one of the numbers (a) and set the first carry in bit to 1 then you have implemented a subtractor, with the a subtracted


4.4 Fast Carry Generation

- **Fast Carry** - Unlike carry adder, doesn't require previous adders to have been completed
- Different Carries
 - Carry Kill - The carry out is always zero, when $k_i = \bar{a}_i.\bar{b}_i$
 - Carry Propagate - The carry is the same as the carry in, when $p_i = a_i \oplus b_i$
 - Carry Generate - The carry our is generated independently of carry in, when $g_i = a_i.b_i$
- The $i + 1^{\text{th}}$ carry is given by $c_{i+1} = g_i + c_i.p_i$

5 Implementing Combinational Logic in Other Ways

 
5.1 ROM

- Read only memory
- Acts like a look up table
- Can be efficient if lots of minterms must be generate, otherwise will have few non-zero entries
- CPU uses address bus to specify location data being read/written to
- Data bus used to convey data too and from location
- A tristate buffer is used to control what can output to a bus



- The following control signals are used
 - OE - Output enable, enable output buffers
 - WE - Write enable, determines whether data is written or read (not for ROM)
 - CS - Chip select, determines if the chip is activated

5.2 PAL

 

- Programmed by selectively removing connections in the AND and OR planes
- These are controlled by fuses or memory bits

6 Components

- **Multiplexor** - Chooses one of many inputs
- **Demultiplexos** - A single input is directed to one output
- **Decoder** - Enables a specific output


7 Sequential Logic

7.1 Excitation and Characteristic Tables

- **Characteristic Table** - Gives the next state of the output given the current inputs and state
- **Excitation Table** - Gives the required inputs to achieve a particular next state given a current state

7.2 Latches

- RS Latch

 


S	R	Q	\bar{Q}
0	0	latch	latch
0	1	0	1
1	0	1	0
1	1	0	0

- Synchronisation:

- Asynchronous - Output changes as a direct result of input changing
- Synchronous - Output only changes as a result of a global enabling signal or clock


- Transparent D Latch

 

D	EN	Q'	\bar{Q}'	comment
X	0	Q	\bar{Q}	RS hold
0	1	0	1	RS reset
1	1	1	0	RS set


- This level triggered
- Is represented using the following symbol

Symbol

 

• **Master-Slave D Flip-Flop**

 - Edge triggered - Q changes with the rising edge of CLK



• **J-K Flip-Flop**

- Extension of a D flip flop
- Has the following state transition table

J	K	Q'	Q̄'	Comment
0	0	Q	Q̄	Hold
0	1	0	1	Reset
1	0	1	0	Set
1	1	Q̄	Q	Toggle

• **T Flip-Flop**

- Extension of a J-K flip flop
- Equivalent to connecting J and K together
- Has the following state transition table


T	Q'	Q̄'	Comment
0	Q	Q̄	Hold
1	Q̄	Q	Toggle

7.3 Sequential Circuits

• **Timing**

- Setup Time - Minimum time that the data must be stable at the input before the clock edge
- Hold Time - Minimum time that the data must remain stable on the flip-flop input after the click edge

- **Ripple Counter**

 


- Not synchronous
- Outputs don't change at the same time
- Propagation delay builds up

- **Synchronous Counter** - Use Global clock signal, use the following steps

- Write down state transition table
- Determine FF excitation table
- Determine the combinations logic necessary to generate the required FF excitation from the current states

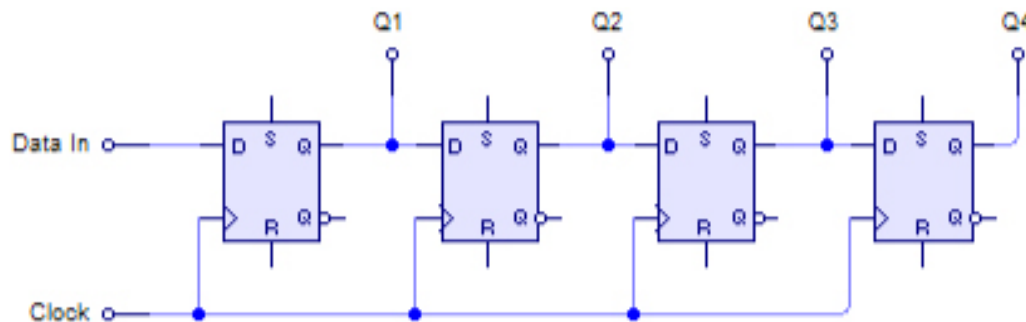- **Shift Register** - Converts serial data into parallel data




7.4 Finite State Machine

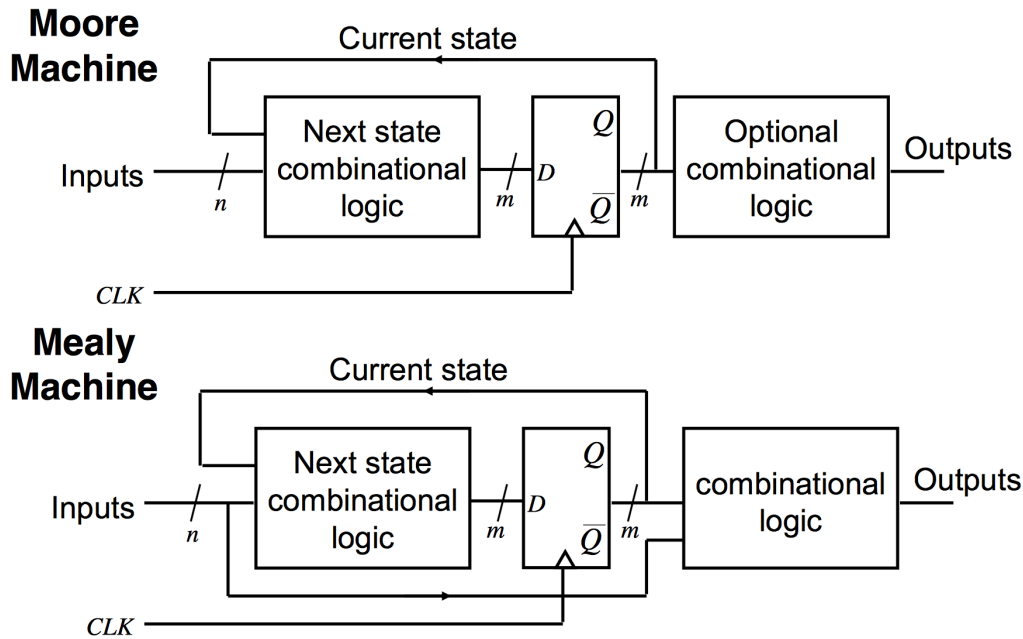7.4.1 Types of Machine

- **Finite State Machines** - Deterministic machine that produces outputs which depends on its internal state and external inputs
- **States** - The set of internal memorised values, shown as circles on the state diagram
- **Inputs** - External stimuli, labelled as arcs on the state diagram
- **Outputs** - Results from the FSM
- **Moore Machines**
 - Output comes directly from clocked flip flops
 - Define logic based on state
- **Mealy Machine**

- Outputs depend upon timing of inputs
- Each transition has Input/Output
- Difference between them



- Mealy must have output logic that uses both the input and state

7.4.2 Implementation

- When designing the machine, ensure that every start up state will eventually reach a valid state
 - If not then use asynchronous clear and preset FF inputs to set to a known state at power up
 - If it does reach a valid start for all start states it is said to self-start
- Wiring complexity can be as bigger issue as gate complexity
- **Storing State**
 - **Sequential State Assignment**
 - * Just count up
 - **Sliding State Assignment**

<i>c</i>	<i>b</i>	<i>a</i>	<i>c'</i>	<i>b'</i>	<i>a'</i>
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	1	1	0
1	1	0	1	0	0
1	0	0	0	0	0

- **Shift Register Assignment**
 - * Output from final shift register is connected to the input of the first
 - * Data continues to cycle through the register

<i>e</i>	<i>d</i>	<i>c</i>	<i>b</i>	<i>a</i>		<i>e'</i>	<i>d'</i>	<i>c'</i>	<i>b'</i>	<i>a'</i>
0	0	0	1	1		0	0	1	1	0
0	0	1	1	0		0	1	1	0	0
0	1	1	0	0		1	1	0	0	0
1	1	0	0	0		1	0	0	0	1
1	0	0	0	1		0	0	0	1	1

– **One Hot State Encoding**

- * Shift register assignment buy with only one flip-flop holds a 1
- * Only one flip-flop has a 1
- * One flip-flop per state
- * Results in simple fast state machines
- * Outputs are generated by ORing together appropriate flip-flop outputs

• State minimisation - Using row matching


– Draw out the state transition table, eg.

Current State	Next State X=0	Next State X=1	Output X=0	Output X=1
A	B	C	0	0
⋮	⋮	⋮	⋮	⋮

- Combine any states with the same next states and outputs
- Repeat until no further combinations can be done

• Can use GAL (generic array logic) devices to implement FSMs

 – Similar to PALs but outputs from OR plane go back into AND plane



- Can use FPGAs (field programmable logic array)
 - A sea of wires controlled by look up tables
 - Look up tables downloaded from memory

8 Electricity

8.1 Electric Laws

- Current is the rate of charge

$$Q = It$$

- Electromotive force is the energy per unit charge provided by a battery

$$V = \frac{E}{Q}$$

- Power is the rate of energy dissipation

$$P = \frac{E}{t} = \frac{QV}{t} = IV$$

- Capacitors store charge

- Charging

$$I = I_0 e^{-\frac{t}{CR}}$$


$$V_{out} = V_{cell} \left(1 - e^{-\frac{t}{CR}} \right)$$

- Discharging

$$V_{out} = V_{cell} e^{-\frac{t}{CR}}$$

 
8.2 Circuit Theory

- Kirchhoff's Current Law - The sum of currents entering a junction is zero
- Kirchhoff's Voltage Law - In any closed loop of an electric circuit the sum of all the voltages in that loop is zero
- Graphical Approach
 - Plot the I-V characteristics of the components, with one starting at the left hand side of the axis, the other on the right
 - Where the cross gives the current and voltages through them, eg.



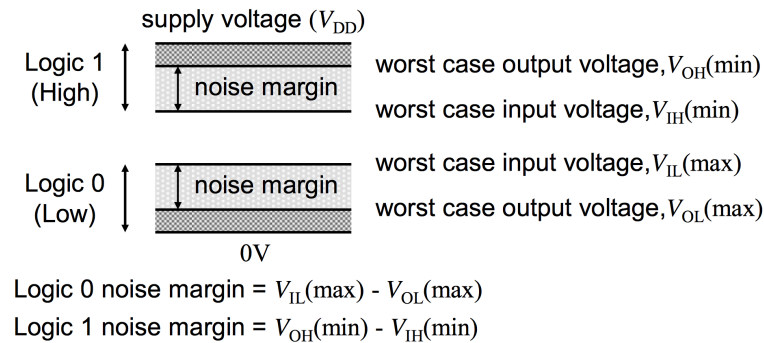8.3 Noise Margin

- The tolerance for noise is quantified in terms of the noise margin




8.4 Semiconductors

- A material with a low electron density
- Silicon is a poor conductor - a semiconductor
 - As temperature rises ($> 0^\circ K$) electrons break bonds and can move freely
- n-type Silicon
 - The silicon is doped with Arsenic, giving it an extra electron
 - This electron will break free and move
 - The free electron will conduct electricity
 - Arsenic is a donor
- p-type Silicon
 - The silicon is doped with boron
 - This leaves a hole, an absent valence electron
 - This hole can move throughout the lattice
 - The hole has a positive charge and therefore causes a flow of current
 - Boron is an acceptor
- p-n Junction
 - n-type and p-type semiconductors are combined
 - The electrons and holes diffuse across junction because of the large concentration gradient
 - Electrons diffusing out of n-type leaves positively charged donor atoms
 - Holes diffusing out of p-type leaves negatively charged acceptor atoms
 - This creates a depleted region, with no holes or electrons, this is the space charge region
 - Depleted region causes an electric field that opposes diffusion
 - Equilibrium reached where no more charges move across junction
 - The field's pd is known as the **contact potential**
- Biased p-n Junction
 - The current through a p-n junction depends on its direction


- **Reverse Bias** - n-type positive
 - * n-type positive, electrons removed, holes removed from p-type
 - * Space charge region and its electric field increased
 - * **Causes a small current**
- **Forward Bias** - n-type negative
 - * n-type negative, electrons pushed towards junction, holes also pushed towards junction in p-type
 - * Space charge region and its electric fields reduced
 - * Diffusion current increases
 - * **Causes a large current**
- This is a diode

9 Transistors

9.1 MOSFET

 


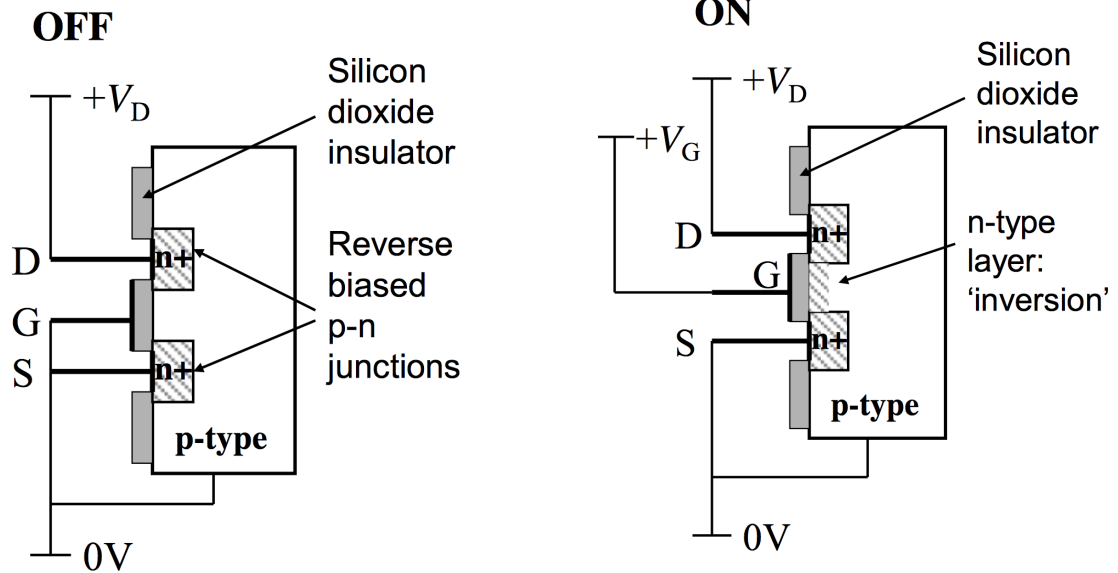- The current flow from D to S is controlled by the voltage applied between G and S (V_{GS})
- When $V_{GS} = 0V$ the transistor is off, $I_{DS} = 0A$
- **n-channel MOSFET**



- When the gate voltage V_g is positive electrons are attracted to G
- This creates an n-type channel and a path from S to D
- Only occurs when V_G is larger than the threshold voltage, typically 0.3 to 0.7V


• p-channel MOSFET

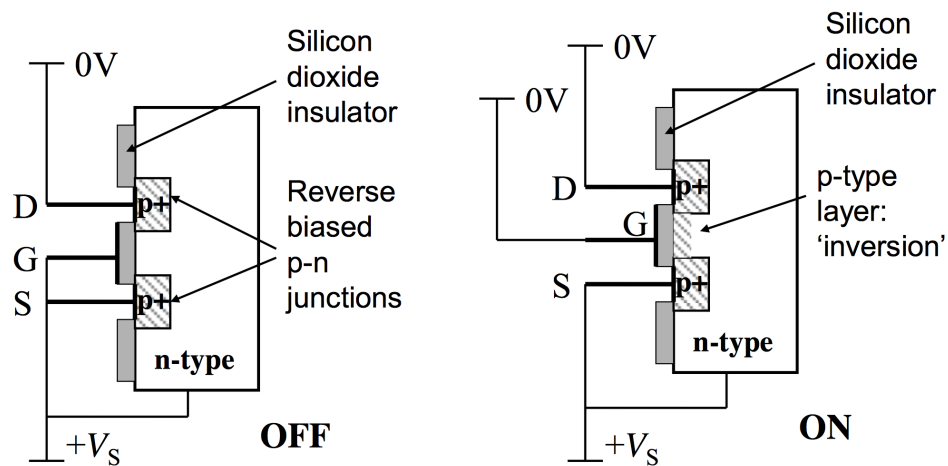


- This is the opposite to an n-channel

 9.1.1 n-MOS Transistors

- MOSFETs can be used to create an n-MOS inverter



 
- This does not have the ideal characteristic the we would want
- n-MOS can be used to make other logic functions (eg. NAND or NOR)
 - It has fundamental problems
 - * Speed of operation
 - * Power consumption
 - Main speed limitation is due to stray capacitance, giving the following graph



- When the transistor is on current follows throw R_1 , dissipating power

 9.1.2 CMOS Logic

- Uses n-channel and p-channel MOS transistors
- CMOS Inverter



- Has much better characteristics than n-MOS inverter
- Only dissipates energy when switching (when both transistors are on)
- Can be used to build logic gates
- Best to stick to one logic family (eg. CMOS, NMOS, ECL, TTL)